

Brac University

Department of Electrical & Electronic Engineering

Summer2026

Course Number : EEE321L

Section :01

Group No :03



9

Junaid (20/7/26)

Lab Report

Experiment no: 04

Name of the experiment:

No-Load Performances of overhead transmission line

Prepared by:

Name: Ruslan Bin Alam ID: 24121091

All Group members:

Sl.	ID	Name
1.	24121205	Souvik Barman Ratul
2.	23221051	Syed Abrar Faiaz
3.	23221150	Elma Eleyah
4.	23221042	Sadia Jahin
5.	24121091	Ruslan Bin Alam

Objective :

(1)

- (i) Measurement of the voltages in no-load operation
- (ii) Concept of operating capacitance
- (iii) Line model with increased operating capacitance

Theoretical Background :

A transmission line is one of the most important components of an electrical power system, responsible for transferring electrical energy from generating station to consumers. No-load operation occurs when the sending end is energized while the receiving end remains open or disconnected from any load. Even though no load current flows, the distributed capacitance of the line

allows a small charging current to circulate, no-load

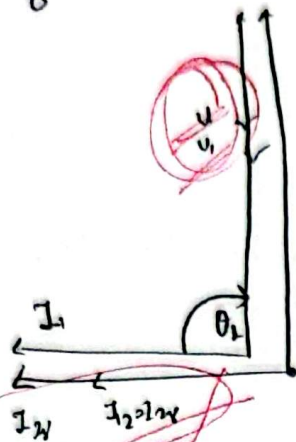



Fig: Single-phase Equivalent circuit Diagram of a Loss-free line in No load operation, with appropriate Vector Diagram.

This charging current produces a voltage rise at the receiving end, known as Ferranti effect, which becomes more noticeable as the transmission line length increases. The experiment demonstrates how line capacitance influences voltage distribution

no-load condition and highlights the importance of considering capacitive effects in transmission system design; voltage regulation and the safe operation of high-voltage power networks.

Apparatus:

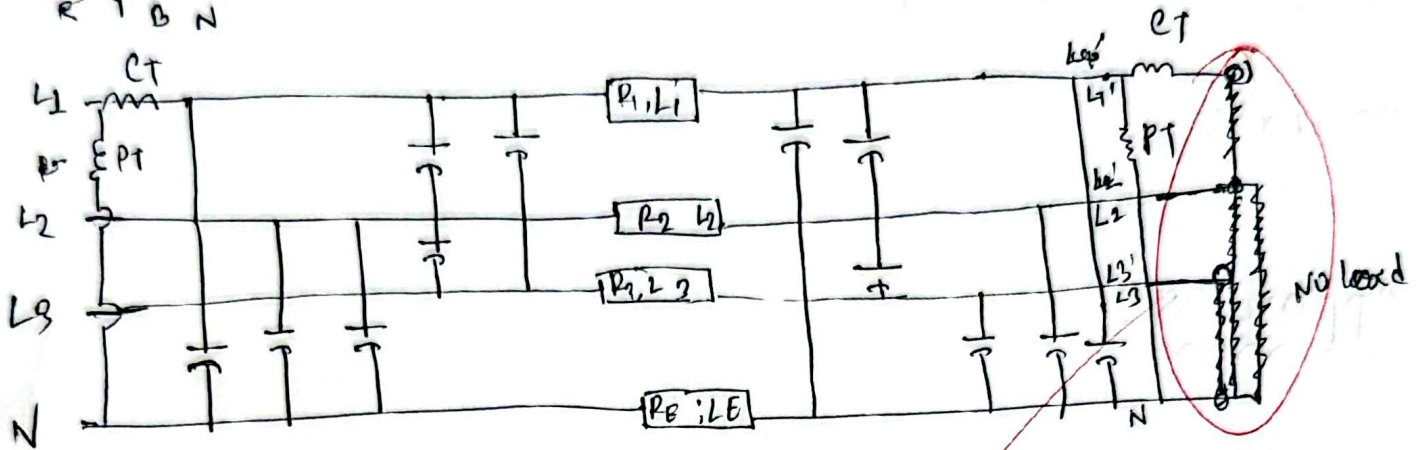1. Three phase supply
2. Overhead Line Model
3. Line Capacitor
4. power Meter
5. Moving-Iron voltmeter



Assemble the circuit per the manual (insert bridging plugs so the model capacitances are connected) set the supply to $U_N = 200 \text{ V}$. and measure the voltages at the beginning and end of the line and active and reactive powers for one phase. Compare the results with those at experiment an equivalent capacitance of the operating capacitance C_B performs in the same way as the individual capacitances C_E and C_L of the line.

Assemble the circuit per the manual (insert bridging plugs so the model capacitances are connected) set the supply to $U_N = 200 \text{ V}$. and measure the voltages at the beginning and end of the line and active and reactive powers for one phase. Compare the results with those at experiment an equivalent capacitance of the operating capacitance C_B performs in the same way as the individual capacitances C_E and C_L of the line.

Hardware Setup:-

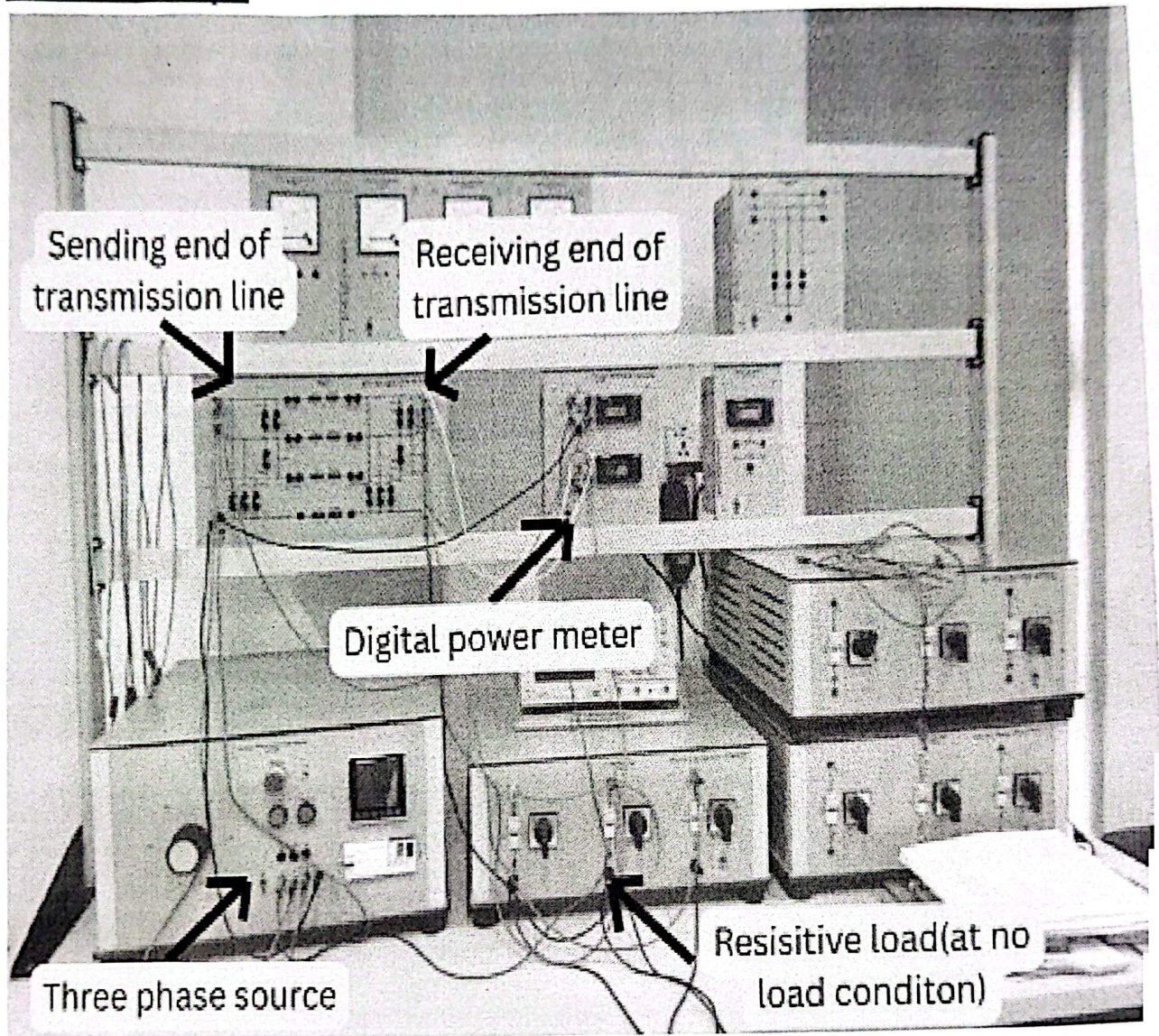


Figure: Hardware setup for no load condition

table :

(3)

	I_1	V_1	P_1	V_2	θ_1
All (5μF) Capacitors	0.254	140.8	1.3	157.6	-34
C_E (2μF)	0.108	140.6	0.4	148.4	-12.3
C_L (3μF)	0.163	140.5	0.8	152.3	-20.9
without Capacitors	0	140.3	0	140.3	0

$$P_c = W C_B V_m^2 = 2 \times \pi \times 50 \times 5 \times 10^{-6} \times 140.8^2 = 31.2$$

Result Analysis :

$$V_1 = 140.8$$

$$P = 1.3$$

$$V_2 = 157.6$$

$$C_B = 5 \mu F$$

$$\theta_1 = -34$$

This experiment result shows that the receiving end voltage increased when capacitors were connected confirming the Ferranti effect. ~~at~~ without any capacitors, both the sending-end and receiving end voltages were almost equal (140.3) and no charging current flowed.

with the 2μF capacitor, the receiving-end voltage increased to 148.4 V with a charging

current of 0.4 A . Using the $3 \mu\text{F}$ cap.
the charging current increased to 0.8 A .
the receiving-end voltage rose to 152.3 . when all,
a capacitors ($5 \mu\text{F}$) were connected, the highest
charging current (1.3 A) and the maximum receiving-
end voltage (157.6 V) were obtained.

These results indicate that increasing the
line capacitance increases the charging current
and cause a greater rise in the receiving-
end voltage. Therefore, the experiment observations
are consistent with the theoretical behavior
of a no-load transmission line and successfully
verify the Ferranti effect

Question & Answer :

$$Q_c = \omega C_3 V_n^2 = 315$$

[from data table calculation]

In no load transmission line, load can operate at a very
low reactive power

This experiment successfully demonstrated the behavior of a transmission line under no-load conditions and verified the Ferranti effect.

The results showed that the receiving-end voltage increased as the line capacitance increased, while the sending-end voltage remained nearly constant. A higher capacitance also produced a larger charging current, which contributed to the voltage rise at the receiving end. Without any capacitor, both voltages were almost equal, confirming that the voltage rise was caused by the capacitive effect of the line. The experime

Observation closely matched the theoretical expectations, although minor differences may have occurred due to instrument inaccuracies, connection losses, and component tolerances. Overall, the experiment provided a clear understanding of the influence of line capacitance on transmission line performance under no load conditions.

Experimental Procedure

Assemble the circuit in accordance with the foregoing topographic diagram.

Remove all bridging plugs connecting the capacitances to line model.

Connect the artificial line capacitances to the beginning and to the end of the line model. Set the supply voltage to $U_N = 200$ V.

Measure the voltage between the outer conductors at the beginning and end of each line capacitance, as well as the reactive power consumed by one of the phases:

$U_1 = \dots\dots\dots$ V $Q = \dots\dots\dots$ Var(cap) $U_2 = \dots\dots\dots$ V

Compare the results with those at experiment 1.1: an equivalent capacitance of the operating capacitance C_B performs in the same way as the individual capacitances C_E and C_L of the line.

Junaid (617126)

Faculty Signature and Date

	I_1	U_1	P	U_2	Q_1
All (54F) Capacitor	0.254	140.8	1.3	157.6	-34
C_E (24F)	0.108	140.6	0.4	148.4	-12.3
C_L (34F)	0.163	140.5	0.8	152.3	-20.9
without Capacitor	0	140.3	0	140.3	0